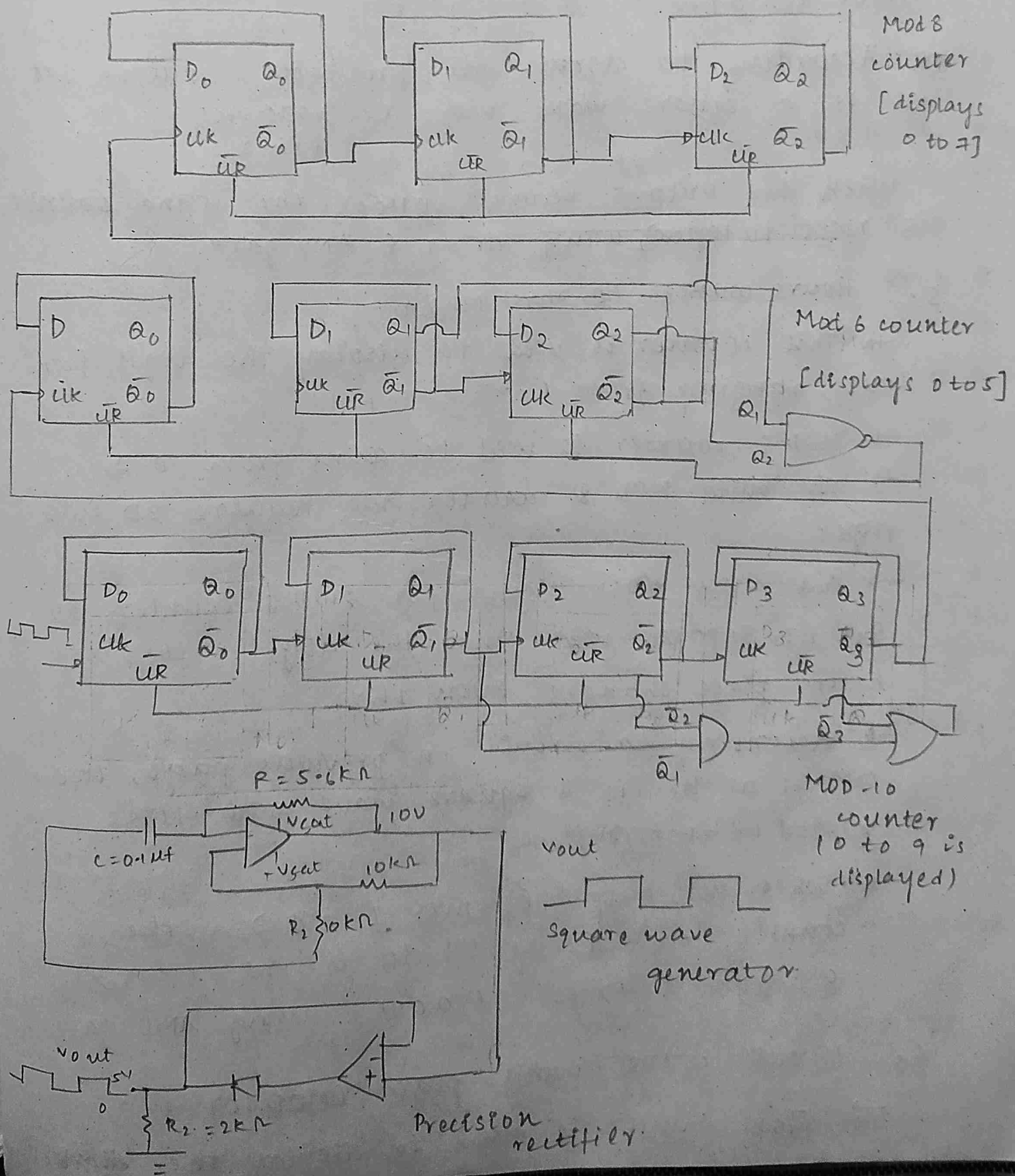


# LAB SESSION-4

Aim of the experiment : To make a digital clock using asynchronous counter which shows until 7 hours 59 minutes from digital 0.

Components :- D flip flops, 7 segment displays, connecting wires, bread board, DC power supply, square wave generator, decoders, 4 input NAND gate, 4 input OR gate, resistors.

Circuit diagram :-



It can also be done using only AND gates.

Theory:

N-11012232 8A.1

1. To build a digital clock showing minutes & hours, we require 4 type of counters, made using D-flip flops

2. Seconds counter (MOD 60) - This counter is required to count seconds, ranging from 0-59 which serves as input clock signal for minutes (unit place) counter

→ To build MOD 60 counter, we require 6 D flipflops and AND gate to count from 0-59 & again reset to 0 sec.

→ According to circuit on previous output at  $Q_{21}$  is a square wave with  $T = 3600 \text{ sec}$  (1hr)

When the output becomes  $(111100)_2$ , the using counter is reset to  $(000000)_2$  using  $dr = 1$  & AND gate.

5. Hours counter (0-7hrs) MOD 8

→ This counter is used to display the digit for hours, ranging from 0-7.

→ MOD 8 counter is used to count from 0-7

→ To build MOD 8 counter, we require 3 D flip flops.

→ The input clock signal for MOD 8 counter is  $Q_{21}$  ( $T = 3600 \text{ sec} = 1 \text{ hr}$ ) since the digit after hours place changes every 1hr

→ According to circuit on previous page, the output at  $Q_5$  is a square wave with time period ( $T = 60 \text{ sec}$ )


→ When the output becomes  $(112'0)_2$ , the counter immediately set to 0, i.e. clear = 1 & output becomes  $(000)_2$  using AND gate.

6. Minutes counter (unit's place) (MOD 10)

→ This counter is used to display the digit

- at units place for minutes ranging from 0-9 min
- MOD 10 counter is used to count from 0-9 min
- To build MOD 10 counter, we require 4 D flip flops & AND gate
- The input clock signal for MOD 10 counter is  $Q_0$  ( $T = 60 \text{ sec}$ ), since the digit changes after every 60 sec.

MOD 10 counter (asynchronous)

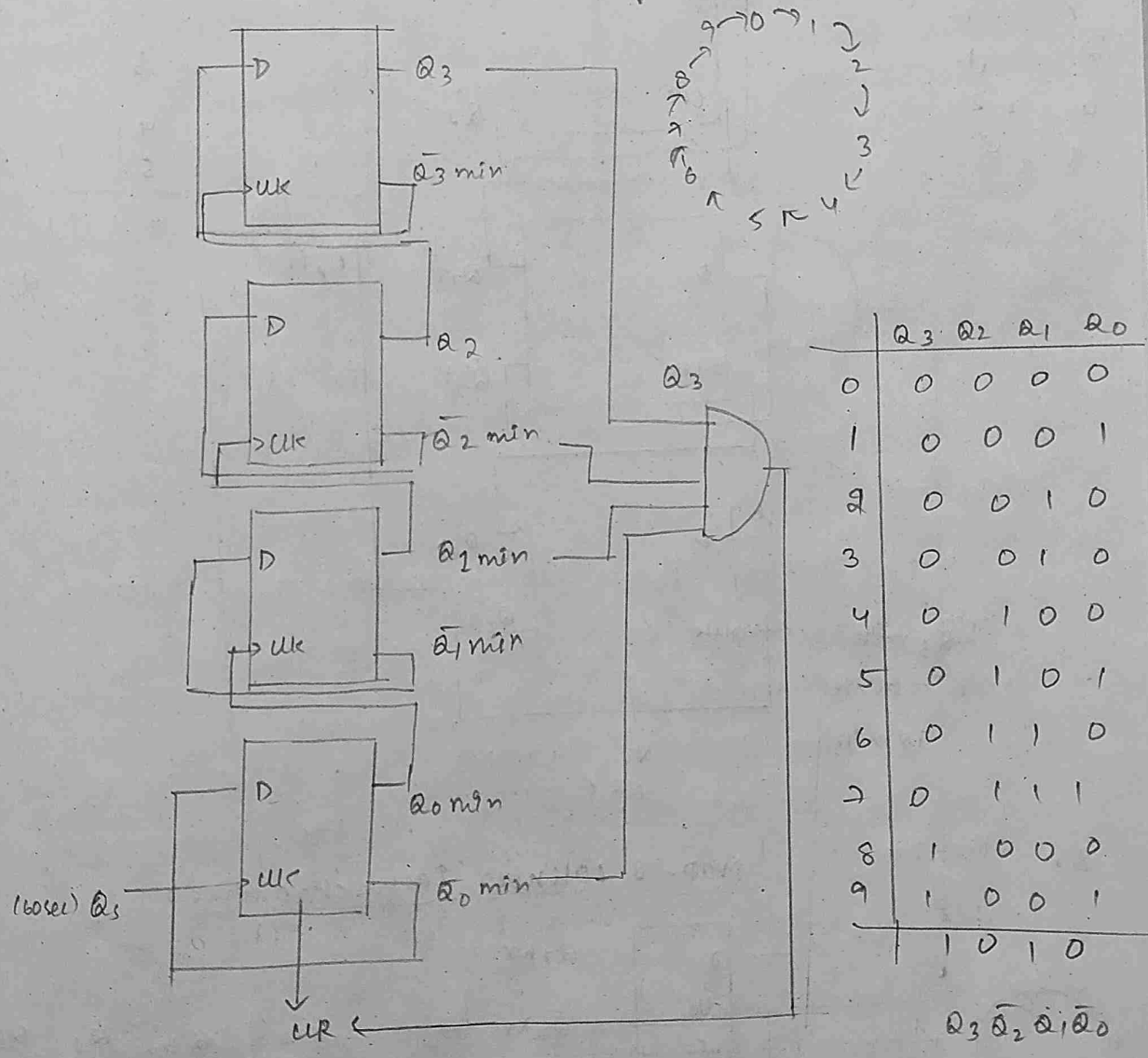

→ According to the circuit on previous page, output at  $Q_0$  min is a square wave with  $T = 60 \text{ sec}$ . when the output becomes 1010, the counter automatically reset to 0000 using  $UR = 1$  by AND gate.


7. Minutes counter (Tens place) (MOD 6)

- This counter is used to display the digit at tens place for minutes, ranging from 0-5
- To build MOD 6 counter, we require 3 D


flip flops & AND gate

→ The input clock signal for mod 6 counter is  $Q_3 \text{ min}$  ( $T = 600 \text{ sec}$ ) since the digit at tens place change after every 10 min (600 sec)

MOD-6 counter (asynchronous)

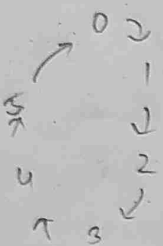

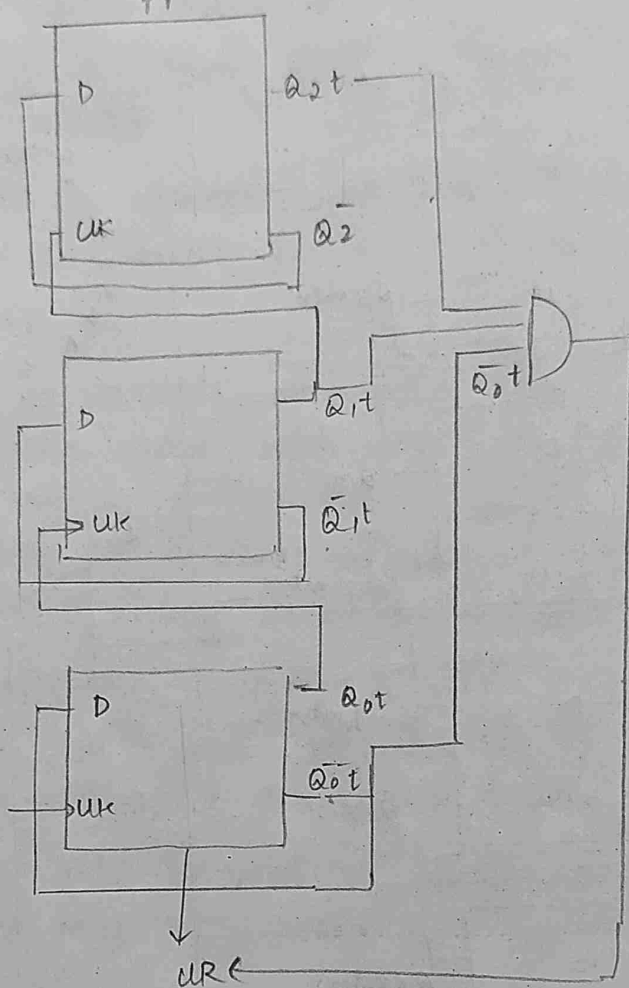$Q_3 \text{ min}$   
( $T = 600 \text{ sec}$   
 $= 10 \text{ min}$ )




	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1


$Q_2 Q_1 \bar{Q}_0$

8.

MOD-8 counter (asynchronous)

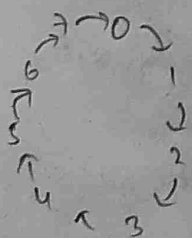


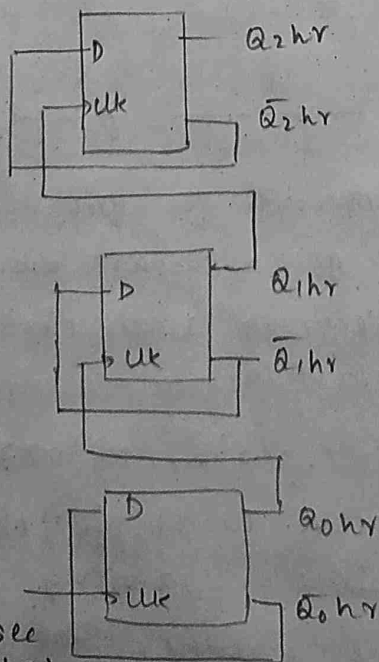$Q_3 \text{ min}$   
( $T = 3600 \text{ sec}$   
 $= 1 \text{ hr}$ )




	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

# MOD-60 counter (asynchronous)

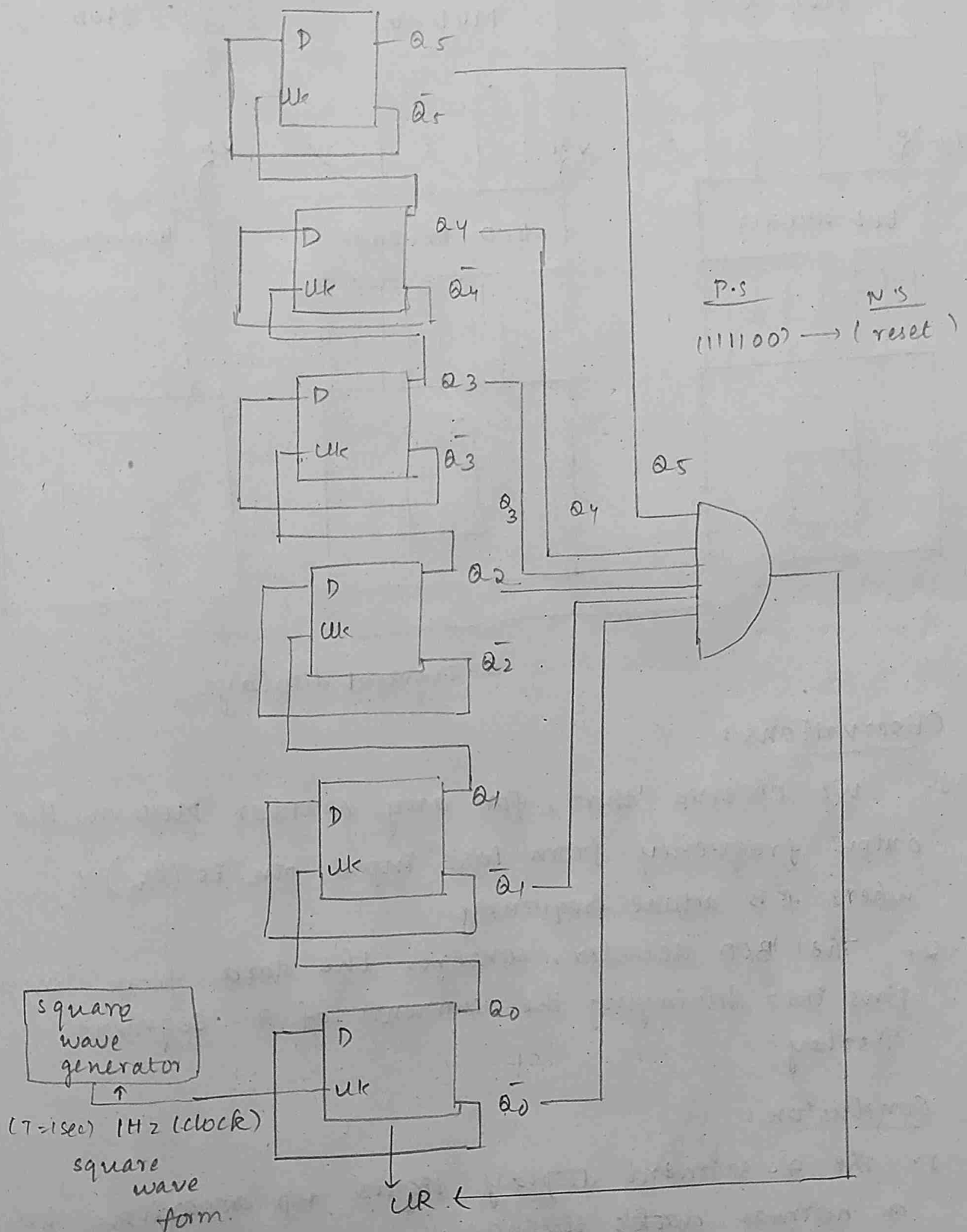

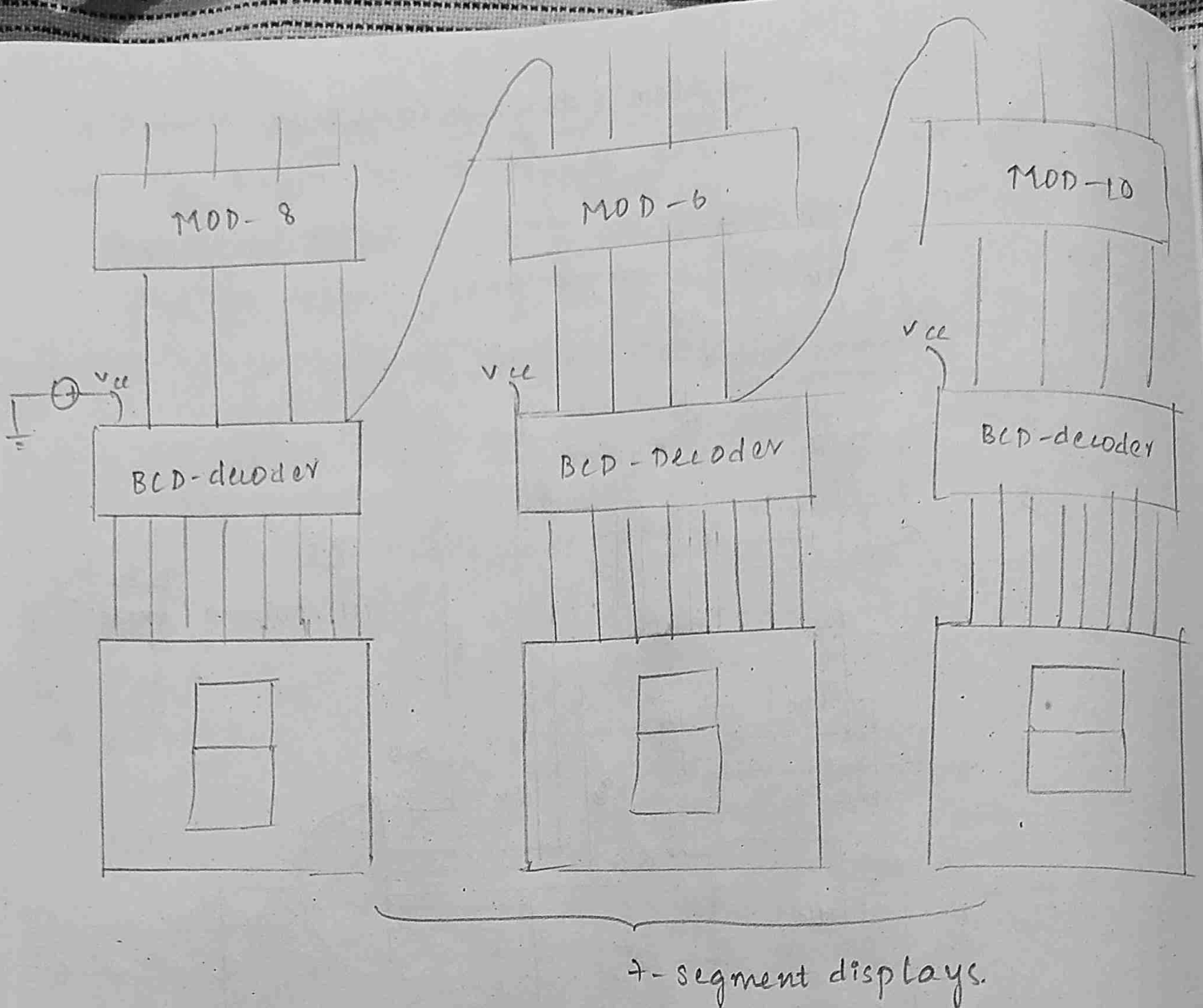10. To display digits

We connect the pins of each counter to BCD 7 segment decoder which is connected to a 7-digit segment LCD display.



### Observations :

1. We observe that, for any counter MOD  $n$ , the output frequency from last input pin is  $(f/n)$ , where  $f$  is actual frequency.
2. The BCD decoder, converts the data from input pins into displaying the segments of 7-segment display.

### Conclusion :

1. The 7-segment display lights up according to a normal clock's timings.
2. Counters work as frequency dividers.



Few snaps of readings

